


Hi Tracy,

This might help with the wave length problem that members in Europe might be having. Is it possible to place it on the Billy dumpit web site?

It works on my radio.

It changes the frequency on Am from division by 10 to division by 9.

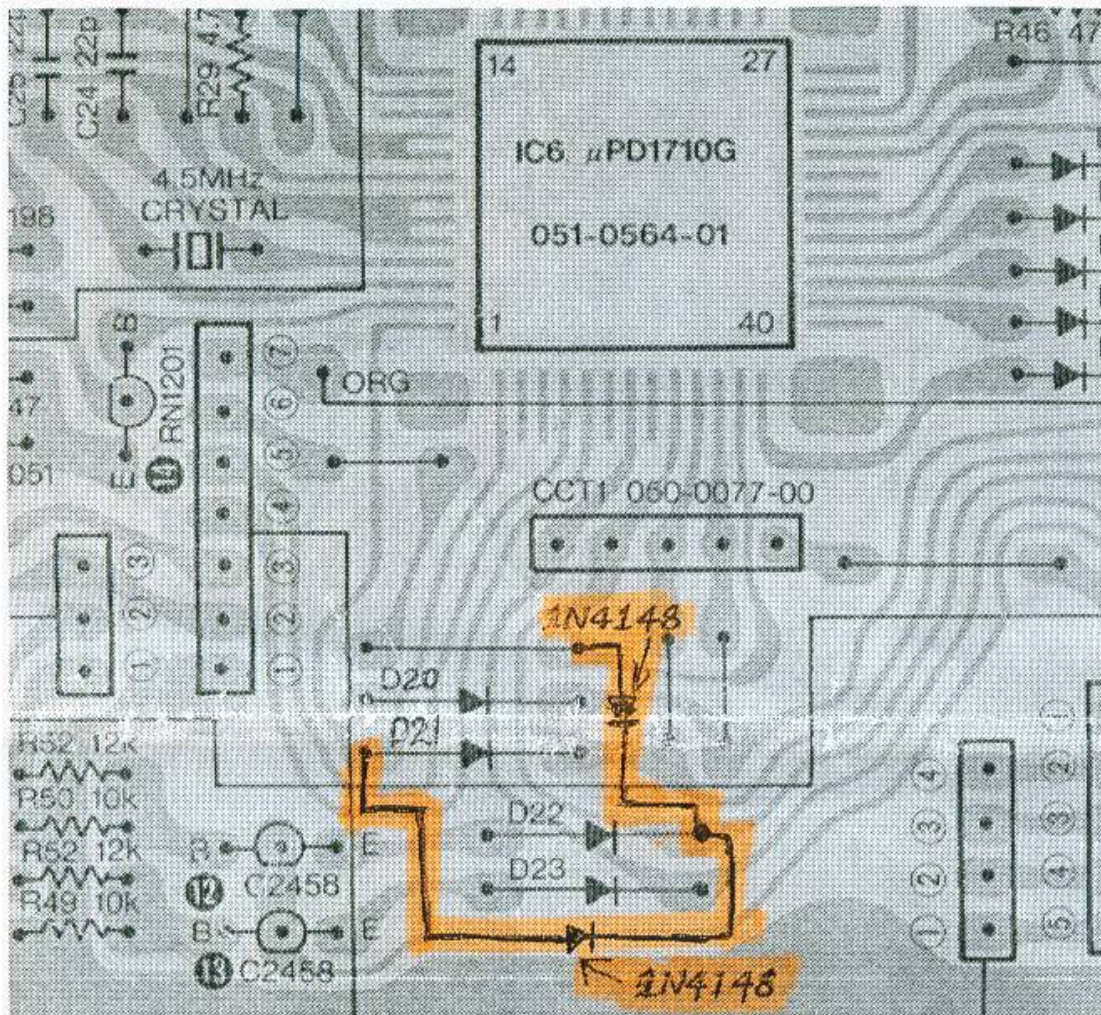My FM also now has .1 increments. The two diodes are 1N4148 and are very cheap.



Dave
UK